
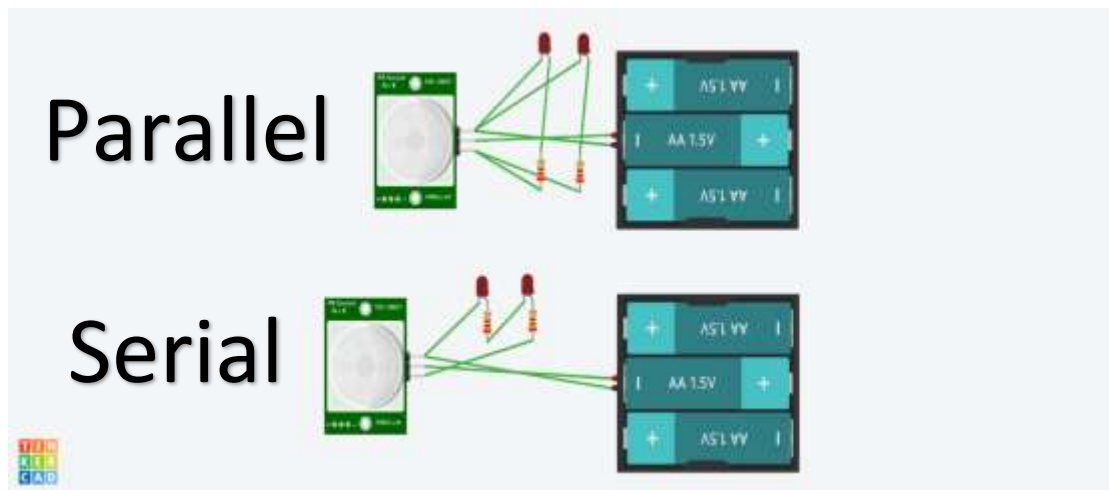


Robot eyes system

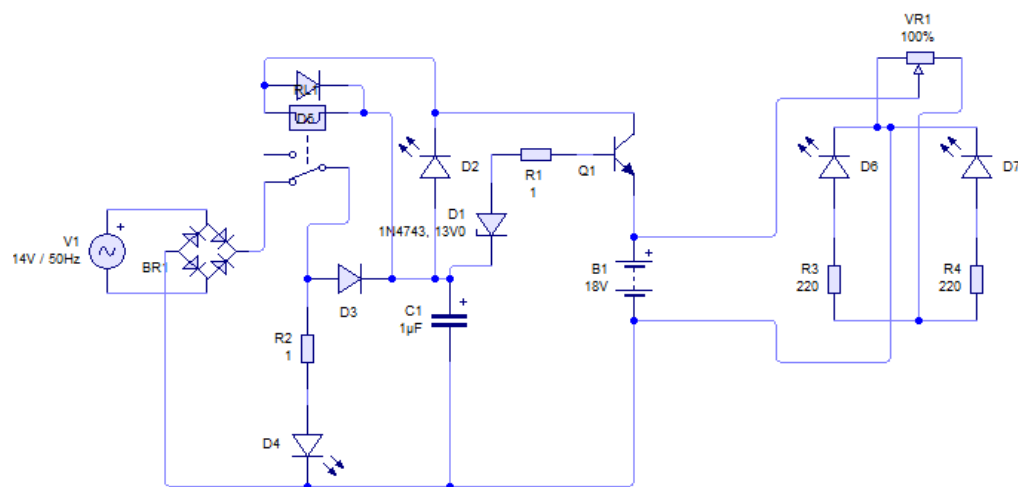

There are two ways to connect the LED eyes in parallel and serial, the parallel contact the voltage source will be equally in both LEDs means they will lite in the same lightness way but if one of them damaged the other one will be ok, unlike then serial the voltage source will division to two-part and if one led been damaged the other will be also damaged too.



In this circuit, you will see the re-charger system for these eyes, I use a potentiometer because in the circuit wizard program there is no PIR sensor, and it works in the same way as the PIR sensor.

Nimah Alyamani

Smartmethod traning program